

Practice Problem

2.2

$$V = IR$$

$$= 3 \times 10$$

$$= 30 \text{ V}$$

$$I = 3 \text{ mA}$$


$$R = 10 \text{ k}\Omega$$

$$G = \frac{1}{R} = \frac{1}{10 \times 1000}$$

$$= 10^{-4} \text{ S} = 100 \mu\text{S}$$

$$P = V \cdot I = 30 \times 3 = 90 \text{ mW}$$

2.5

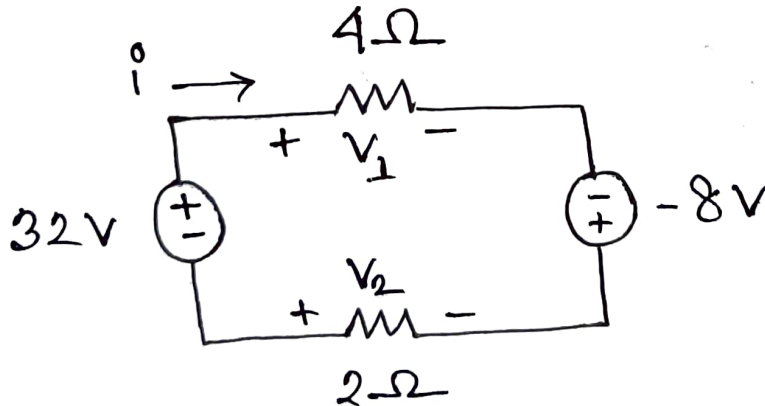

Let current i flows through the loop in clockwise direction.

From Ohm's Law,

$$V_1 = 4i$$

$$V_2 = -2i$$

Applying KVL around the loop,

$$V_1 - (-8) - V_2 - 32 = 0$$

$$\Rightarrow 4i^\circ + 8 - (-2i^\circ) - 32 = 0$$

$$\Rightarrow 6i^\circ = 24$$


$$\therefore i^\circ = 4$$

$$\therefore i^\circ = 4 \text{ A}$$

$$\therefore V_1 = 4 \times 4 = 16 \text{ V}$$

$$\therefore V_2 = (-2) \cdot (4) = -8 \text{ V}$$

2.6

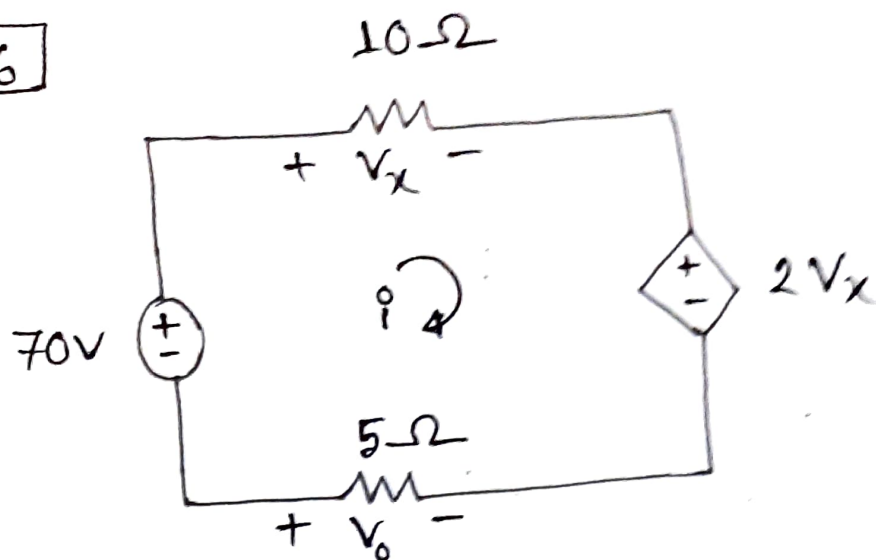

Applying Ohm's Law to 10Ω and 5Ω resistors we get,

$$V_x = 10i$$

$$V_0 = -5i$$

Applying KVL around the loop gives,

$$V_x + 2V_x - V_0 - 70 = 0$$

$$\Rightarrow 3(10i) - (-5i) = 70$$


$$\Rightarrow 35i = 70$$

$$\therefore i = 2$$

$$\therefore V_x = 10 \times 2 = 20 \text{ V}$$

$$\therefore V_o = (-5) \times 2 = -10 \text{ V}$$

2.7

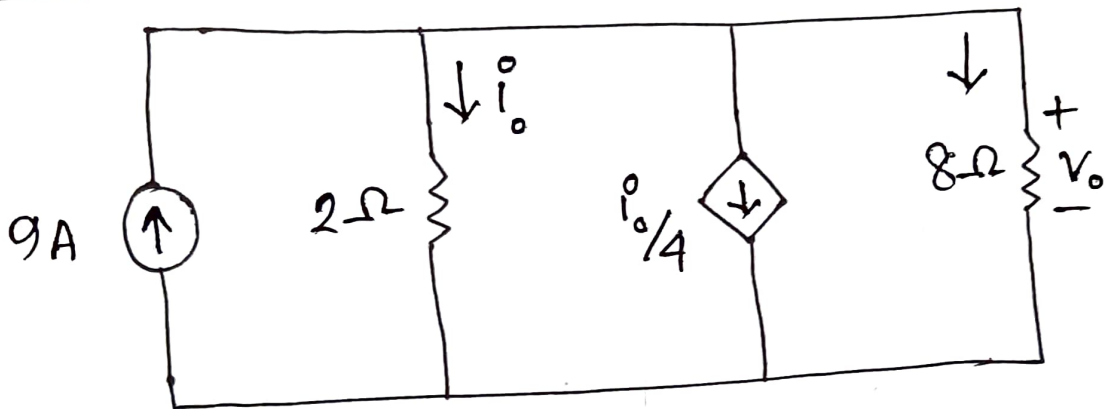

As 2Ω and 8Ω resistors are parallel, so ~~same voltage~~ there is same voltage across them, so,

$$V_o = 2i_o$$

Applying KCL,

$$9 = i_o + \frac{i_o}{4} + \frac{V_o}{8}$$

$$\Rightarrow 9 = i_0 + \frac{i_0}{4} + \frac{2i_0}{8}$$

$$\Rightarrow 9 = \frac{4i_0 + i_0 + i_0}{4}$$


$$\Rightarrow 9 = \frac{6i_0}{4}$$

$$\Rightarrow i_0 = \frac{4 \times 9}{6}$$

$$\therefore i_0 = 6 \text{ A}$$

$$\therefore V_0 = 2 \times 6 = 12 \text{ V}$$

2.8

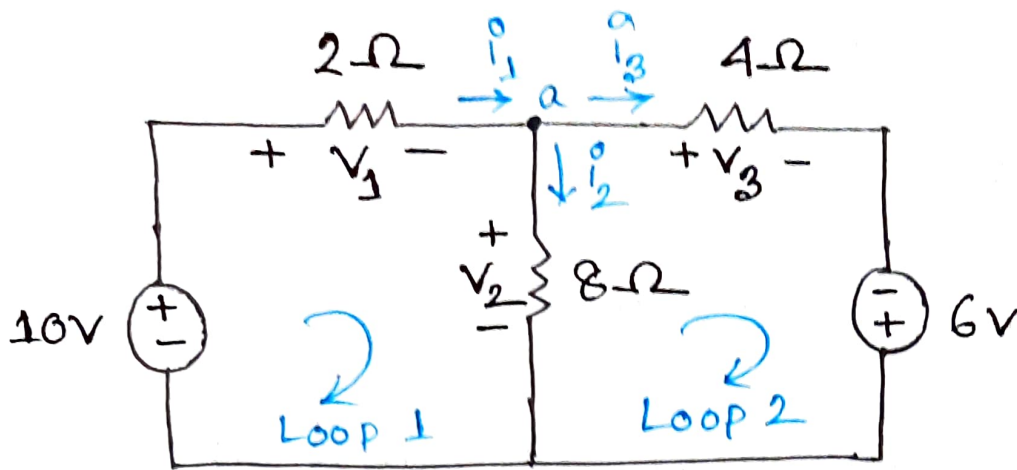

Applying Ohm's Law,

$$V_1 = 2i_1, \quad V_2 = 8i_2, \quad V_3 = 4i_3$$

Applying KCL at node a,

$$i_1 = i_2 + i_3$$

$$\Rightarrow \frac{V_1}{2} = \frac{V_2}{8} + \frac{V_3}{4}$$

$$\Rightarrow 4V_1 = V_2 + 2V_3$$

$$\Rightarrow 4V_1 - V_2 - 2V_3 = 0 \quad \text{--- (1)}$$

Applying KVL to loop 1,

$$V_1 + V_2 - 10 = 0$$

$$\Rightarrow V_1 = 10 - V_2 \quad \text{--- (2)}$$

Applying KVL to loop 2,

$$V_3 - 6 - V_2 = 0$$

$$\Rightarrow V_3 = 6 + V_2 \text{ --- (3)}$$

Substituting eqs. (2) and (3) into

eq. (1) gives,

$$4(10 - V_2) - V_3 - 2(6 + V_2) = 0$$

$$\Rightarrow 40 - 4V_2 - V_3 - 12 - 2V_2 = 0$$

$$\Rightarrow 28 = 7V_2$$

$$\therefore V_2 = 4 \text{ V}$$

Putting this value to eqs. (2) and

(3) gives,

$$V_1 = 10 - 4 = 6 \text{ V}$$


$$V_3 = 6 + 4 = 10 \text{ V}$$

$$\therefore I_1 = \frac{V_1}{2} = \frac{6}{2} = 3 \text{ A}$$

$$\therefore I_2 = \frac{V_2}{8} = \frac{4}{8} = 0.5 \text{ A}$$


$$\therefore I_3 = \frac{V_3}{4} = \frac{10}{4} = 2.5 \text{ A}$$

2.9

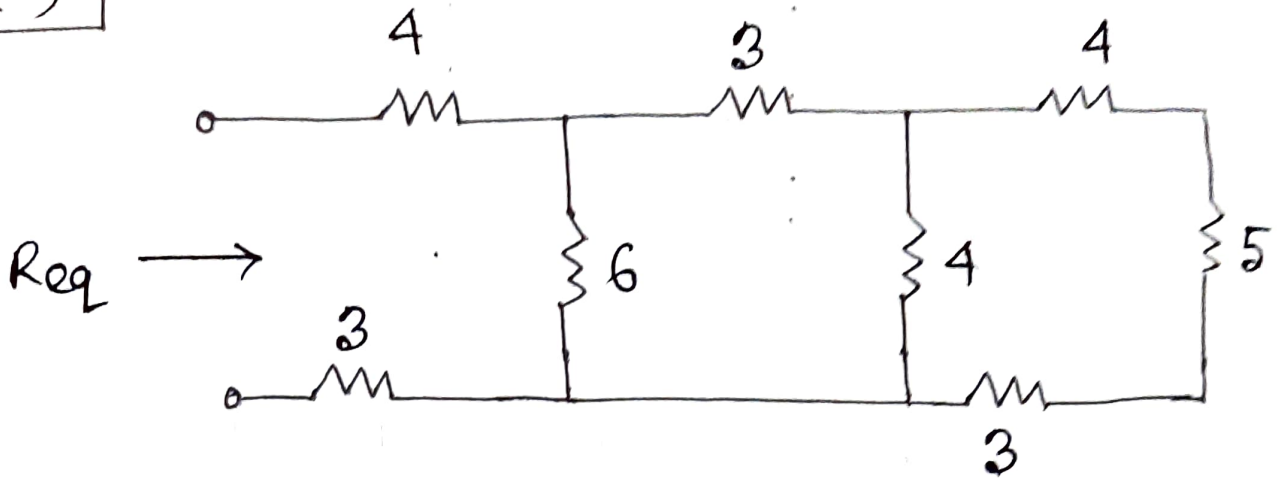

Here, 4Ω , 5Ω and 3Ω resistors are in series,


$$4 + 5 + 3 = 12\Omega$$

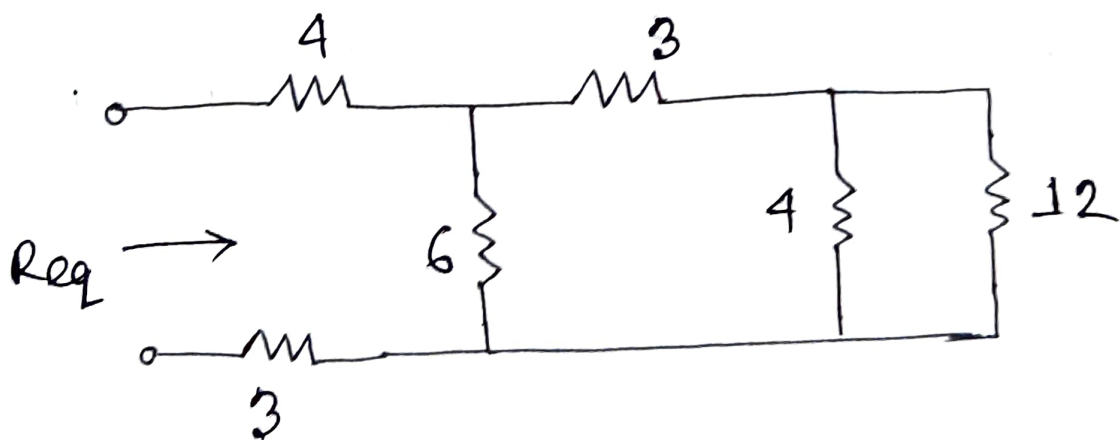

4Ω and 12Ω resistors are in parallel,

$$4 \parallel 12 = \frac{4 \times 12}{4 + 12}$$


$$= 3\Omega$$

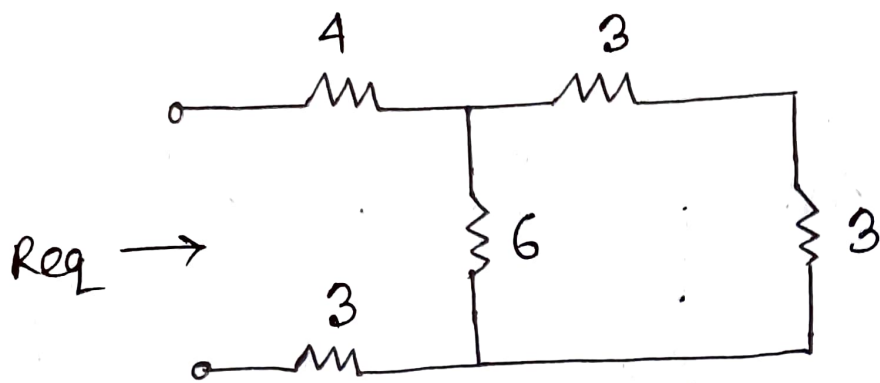

3Ω and 3Ω resistors are in parallel, & series,


$$3 + 3 = 6\Omega$$

6Ω and 6Ω resistors are in parallel,

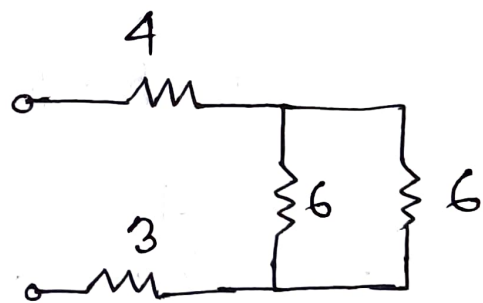


$$6 \parallel 6 = \frac{6 \times 6}{6 + 6} = 3\Omega$$

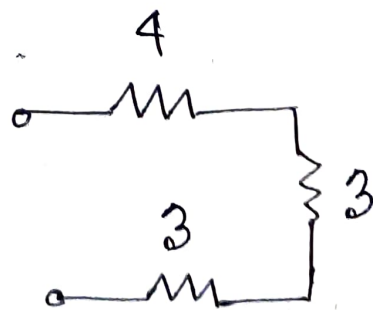Now, 4Ω , 3Ω and 3Ω resistors are in series,



$$\therefore R_{eq} = 4 + 3 + 3 = 10\Omega$$

2.11

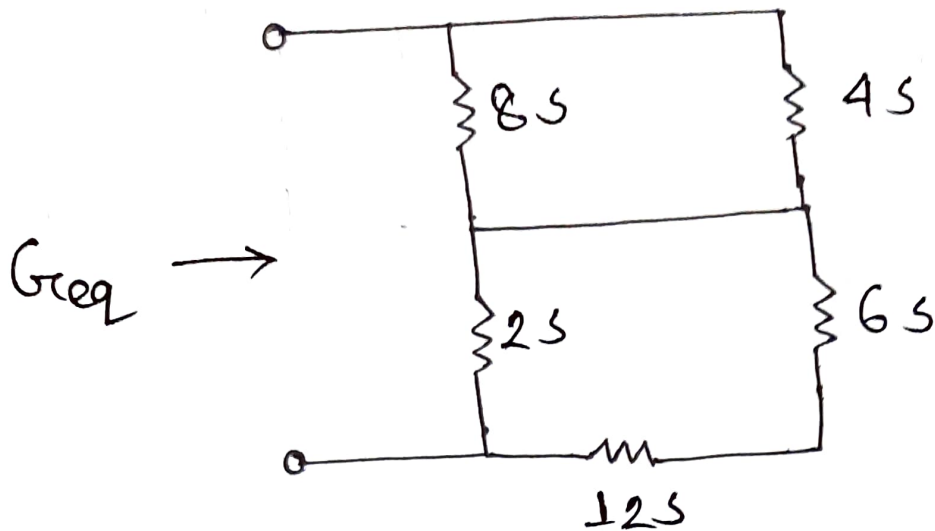


Here $6S$ and $12S$ ~~are~~ are in series,

$$\frac{12 \times 6}{12 + 6} = 4S$$

Here $8S$ and $4S$ are in parallel,

$$8 + 4 = 12S$$

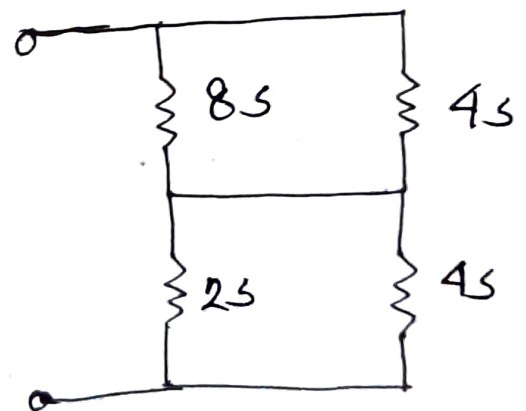


And $2S$ and $4S$ are in parallel,

$$2 + 4 = 6S$$


Now, 12s and 6s
are in series,

$$\therefore G_{eq} = \frac{12 \times 6}{12 + 6}$$

$$= 4s$$

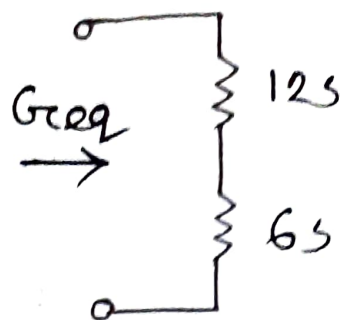


2.10

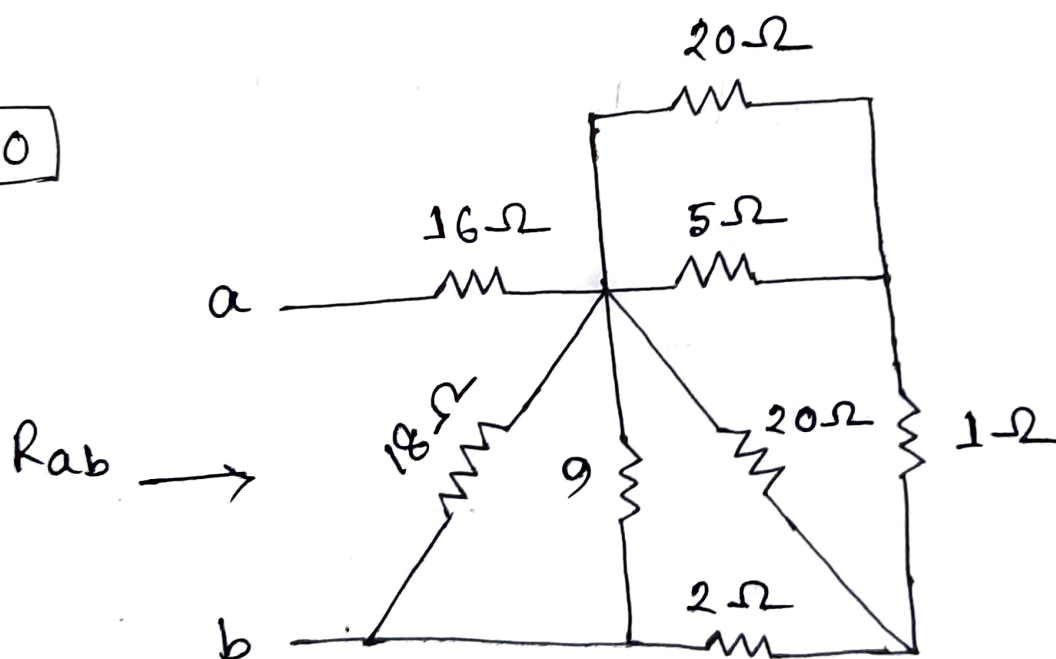


Here, 20 Ω and 5 Ω are in parallel,
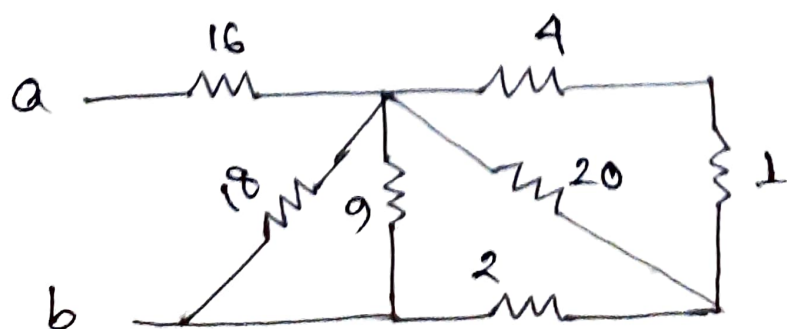
$$20 \parallel 5 = \frac{20 \times 5}{20 + 5} = 4 \Omega$$




$4\ \Omega$ and $1\ \Omega$ are in series,

$$4 + 1 = 5\ \Omega$$

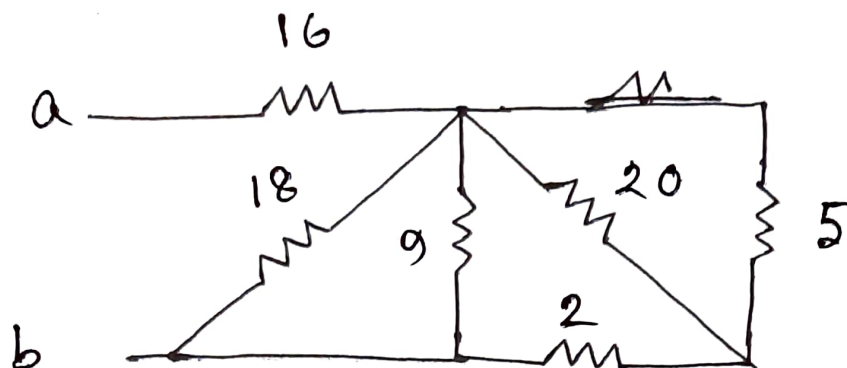

$5\ \Omega$ and $20\ \Omega$ are in ^{parallel,} ~~series~~
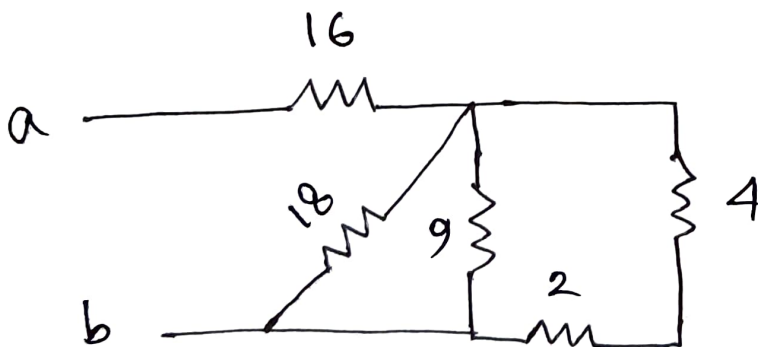
$$20 \parallel 5 = \frac{20 \times 5}{20 + 5} = 4\ \Omega$$



$4\ \Omega$ and $2\ \Omega$ are in series, and



$18\ \Omega$ and $9\ \Omega$ are in parallel,

$$2 + 4 = 6\ \Omega$$

$$9 \parallel 18 = \frac{9 \times 18}{9 + 18} = 6\ \Omega$$

6Ω and 6Ω are
in parallel,

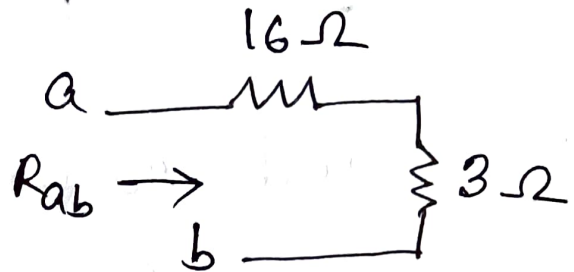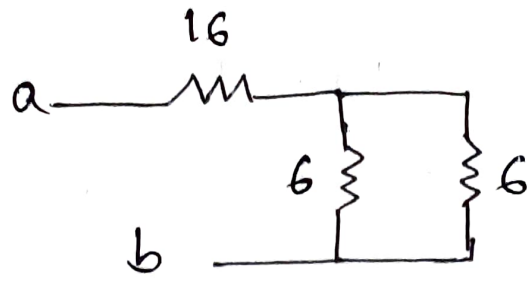
$$6 \parallel 6 = \frac{6 \times 6}{6 + 6} \\ = 3\Omega$$



16Ω and 3Ω resistors are
in series,

$$R_{ab} = 16 + 3 \\ = 19\Omega$$

2.12

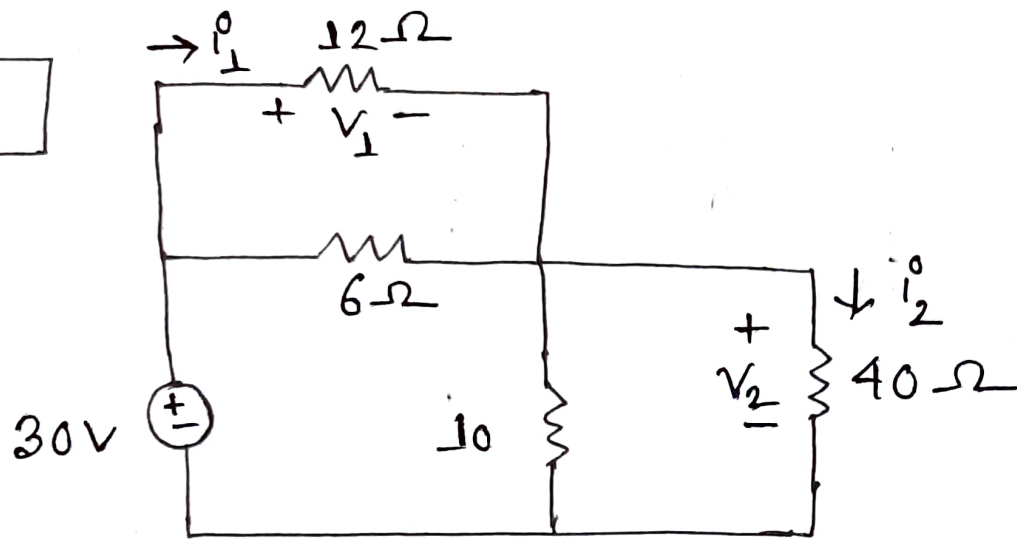

Applying Ohm's Law to 12Ω and 40Ω resistors,


$$i_1 = \frac{V_1}{12}$$

$$i_2 = \frac{V_2}{40}$$

Here 12Ω and 6Ω resistors are in parallel, and 10Ω and 40Ω resistors are in parallel, so,

$$12 \parallel 6 = \frac{12 \times 6}{12 + 6} = 4\Omega$$
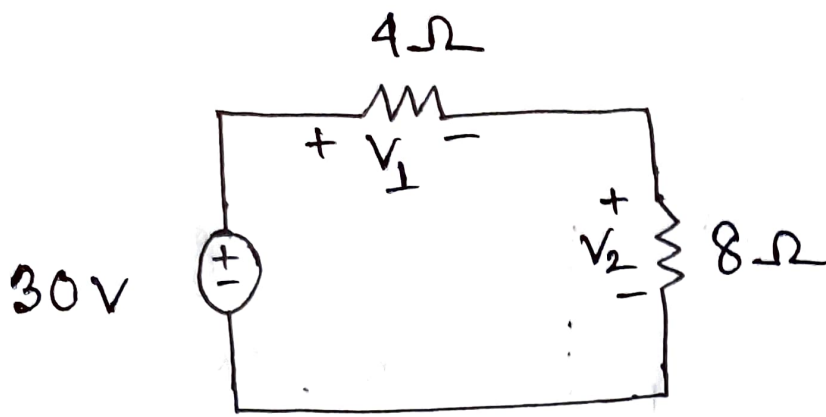
$$10 \parallel 40 = \frac{10 \times 40}{10 + 40} = 8\Omega$$



Applying voltage division rule,

$$V_1 = \frac{4}{4+8} \times 30 = 10V$$

$$V_2 = \frac{8}{4+8} \times 30 = 20V$$

$$\therefore i_1 = \frac{10}{12} = 0.833A$$

$$\therefore i_2 = \frac{20}{40} = 0.5A$$

$$\therefore P_1 = V_1 i_1 = 10 \times 0.833 = 8.33W$$

$$\therefore P_2 = V_2 i_2 = 20 \times 0.5 = 10W$$